

North South University
Department of Electrical & Computer Engineering
LAB REPORT

Course Name: **CSE332L**

Experiment No: 04

Experiment Name: **Design of a 4-bit Binary Up-Down counter**

Report Submission Date: 28.03.21

Section: 11

Student Name: **Hasibul Hossain**

Score

Student ID: **1821534042**

Remarks:

LAB-04: Design of a 4-bit Binary Up-Down counter

Objectives:

Bidirectional counters are capable of counting in either the up direction or the down direction through any given count sequence


As well as counting “up” from zero and increasing or incrementing to some preset value, it is sometimes necessary to count “down” from a predetermined value to zero allowing us to produce an output that activates when the zero count or some other pre-set value is reached. In the 4-bit counter above the output of each flip-flop changes state on the falling edge (1-to-0 transition) of the CLK input which is triggered by the Q output of the previous flip-flop, rather than by the Q output as in the up-counter configuration. As a result, each flip-flop will change state when the previous one changes from 0 to 1 at its output, instead of changing from 1 to 0.

A counter that follows the binary number sequence is called a binary counter. A 4-bit binary counter is a register of 4 flip-flops and associated gates that follows a sequence of states according to the binary count of 4 bits, from 0 to 15. We assume that the LSB is always complemented on every state. The sequence works on the fact that the next significant bit will be complemented only when a previous bit makes a transition from 1 to 0. For example, in case of transition from binary 0011 to 0100(4 to 5), 3rd bit does transition from 0 to 1. So, the 4th bit isn't complemented.

Apparatus:

- 1.4 D-Flip Flop, 4 X-OR gates, 4 OR gate and 7 AND gate.
- 2.Wires for connection.
- 3.Clock

Logic Diagram:

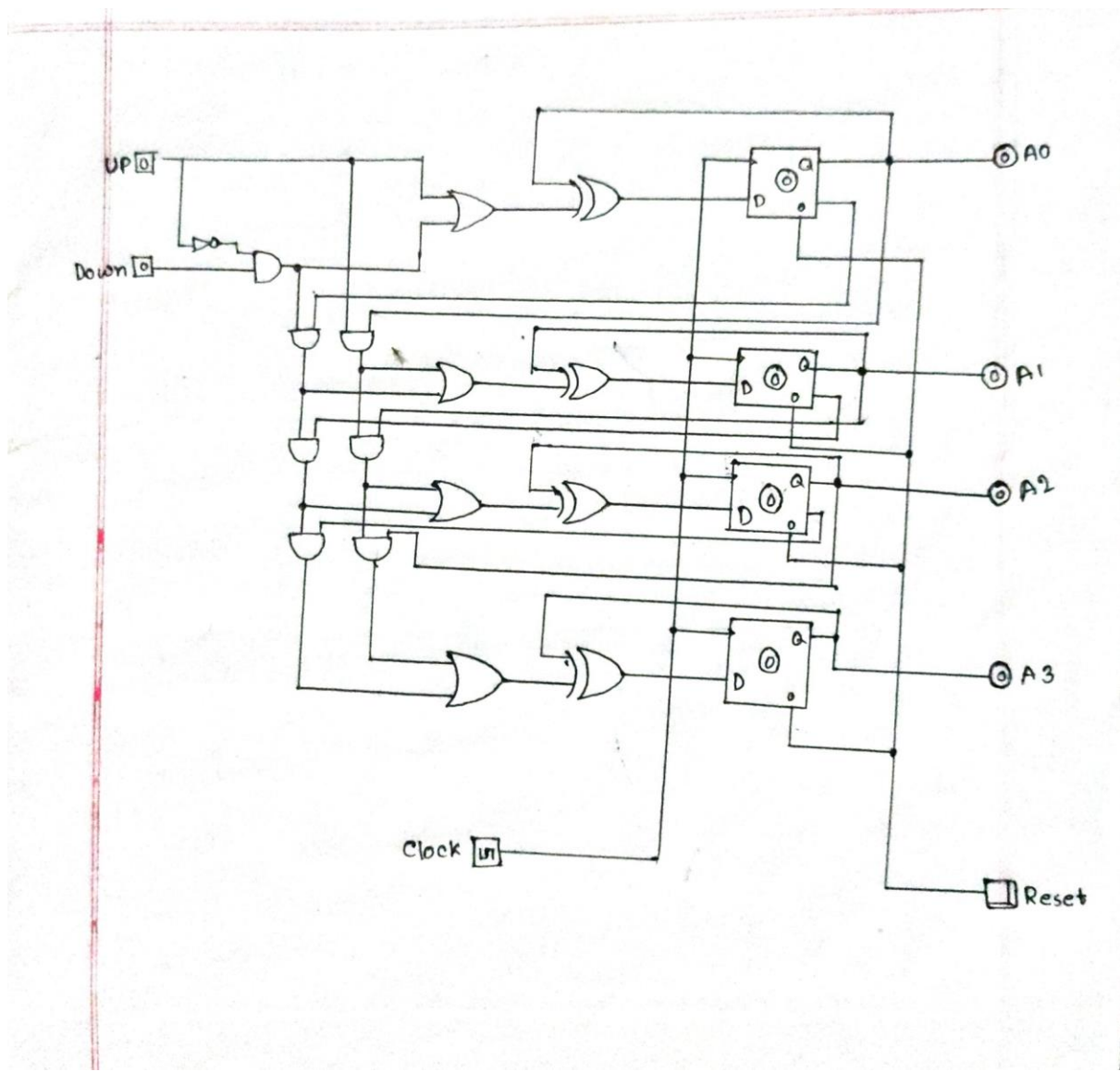

Truth Table:

Clock pulse	A	B	C	D
P0	0	0	0	0
P1	0	0	0	1
P2	0	0	1	0
P3	0	0	1	1

P4	0	1	0	0
P5	0	1	0	1
P6	0	1	1	0
P7	0	1	1	1
P8	1	0	0	0
P9	1	0	0	1
P10	1	0	1	0
P11	1	0	1	1
P12	1	1	0	0
P13	1	1	0	1
P14	1	1	1	0
P15	1	1	1	1

Procedure:

1. There are 4 D-Flip Flop, 4 X-OR gates, 4 OR gates, 7 AND gates, 2 input and 4 outputs.
2. At first, the up-counter input and the down-counter input with a (NOT) gate and (AND) are connected with a OR gate.
3. The output of the OR gate is connected to the input of the X-OR gate and the output is connected with the D-Flip Flop.
4. Then the two AND gates are connected with the up and down counter and the one port the first AND gate is connected with D-Flip Flop and the other one with the X-OR gate.
5. And the input of the X-OR gate is connected with the output of D-Flip Flop will also give the Output A0.
6. There are clock and reset button with the 4 D-Flip Flops.
7. So, the other 3 D-Flop Flops are connected with the remaining gates by the same procedure will give us the outputs A1, A2 and A3.

Logisim:

