

**North South University**  
Department of Electrical & Computer Engineering

**LAB REPORT**

Course Name: CSE332L

Experiment Number: **03**

Experiment Name: **Design of a 4-bit Universal Shift Register**

Experiment Date: 22/03/2021

Report Submission Date: 17/03/2021

Faculty: SFM

Submitted to: Md Saidur Rahman

Section: 06

Student Name: **Koushik Banerjee**

Score

Student ID: **1812171642**

Remarks:

## **Title: Design of a 4-bit Universal Shift Register**

### **Objectives:**

- ❖ Designing a Design of a 4-bit Universal Shift Register by using Logisim software.
- ❖ Learn how to work with Shift Register.


### **Types of equipment:**

- \*Four D Flip Flops (Two 7474 ICs)
- \* Four 4X1 MUX (Two 74153 ICs)
- \* Trainer Board
- \* Wires
- \* Power Supply

### **Function Table:**

S1	S0	Operation	I4	I3	I2	I1	A4	A3	A2	A1
0	0	No change	0	1	1	0	A4	A3	A2	A1
0	1	SHR	1	1	0	0	S1(R)	A4	A3	A2
1	0	SHL	1	1	0	0	A3	A2	A1	S1(L)
1	1	Parallel load	1	1	0	0	1	1	0	0


The diagram illustrates a 4-bit serial shift register implemented using four D flip-flops (labeled  $F_4, F_3, F_2, F_1$ ) and four 4x1 multiplexers (MUX). The flip-flops are connected in a chain where the output of one flip-flop is the input to the next. The inputs to the flip-flops are labeled  $A_4, A_3, A_2, A_1$ . The outputs of the flip-flops are labeled  $I_4, I_3, I_2, I_1$ . The inputs to the MUXes are labeled  $S_1, S_0$ . The outputs of the MUXes are labeled  $I_4, I_3, I_2, I_1$ . The MUXes are connected such that the output of one MUX is the input to the next. The inputs to the MUXes are labeled  $S_1, S_0$ . The outputs of the MUXes are labeled  $I_4, I_3, I_2, I_1$ . The MUXes are connected such that the output of one MUX is the input to the next. The inputs to the MUXes are labeled  $S_1, S_0$ . The outputs of the MUXes are labeled  $I_4, I_3, I_2, I_1$ .

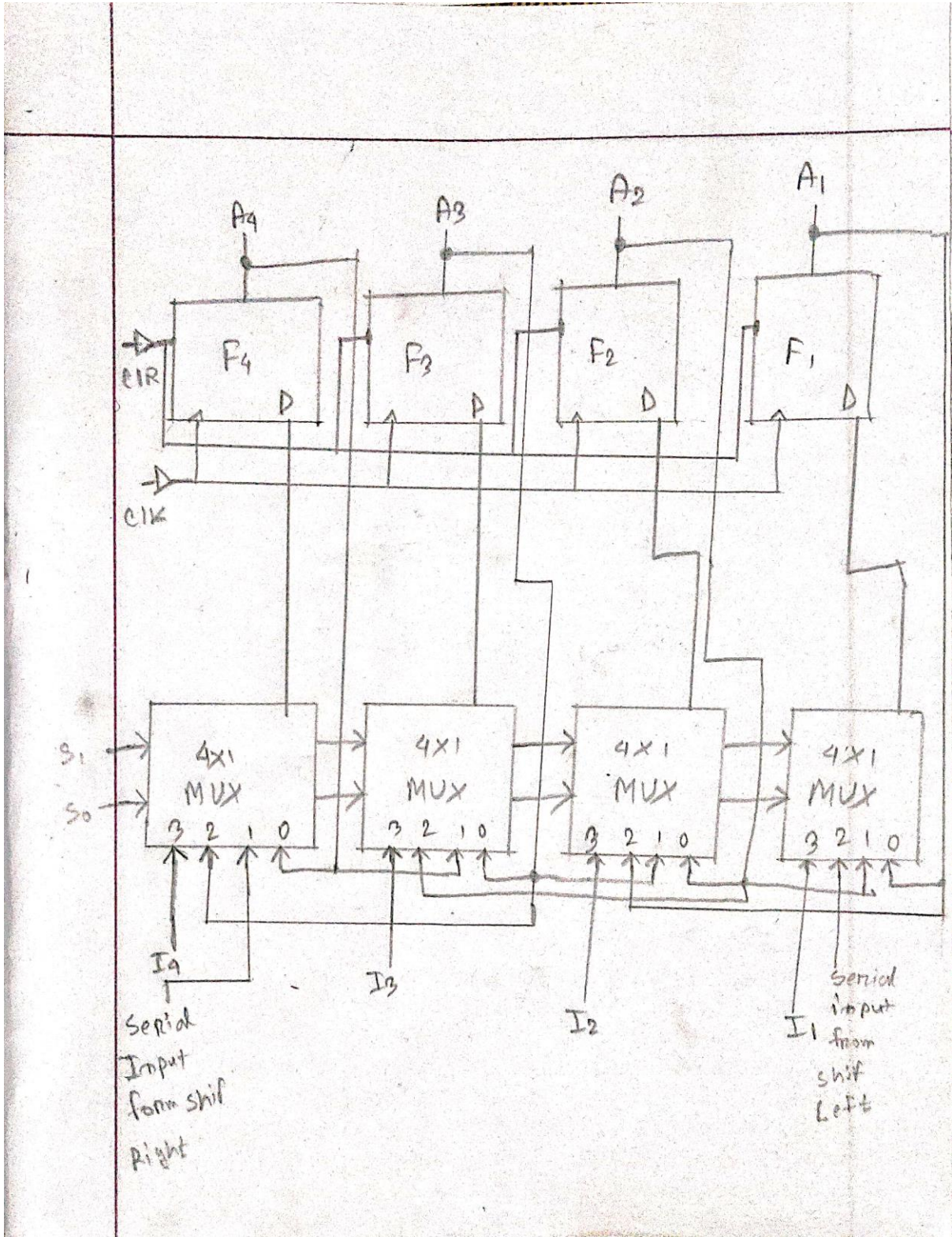

## Procedure:

- 1) Place the ICs on the trainer board.
- 2) Connect Vcc and ground to the respective pins of IC.
- 3) Connect the inputs with the switches and the outputs (A1-A4) with LEDs.
- 4) Apply various combinations of inputs and observe the outputs.
- 5) Verify the experimental outputs with the Function Table.

## Logisim works screenshot(s):

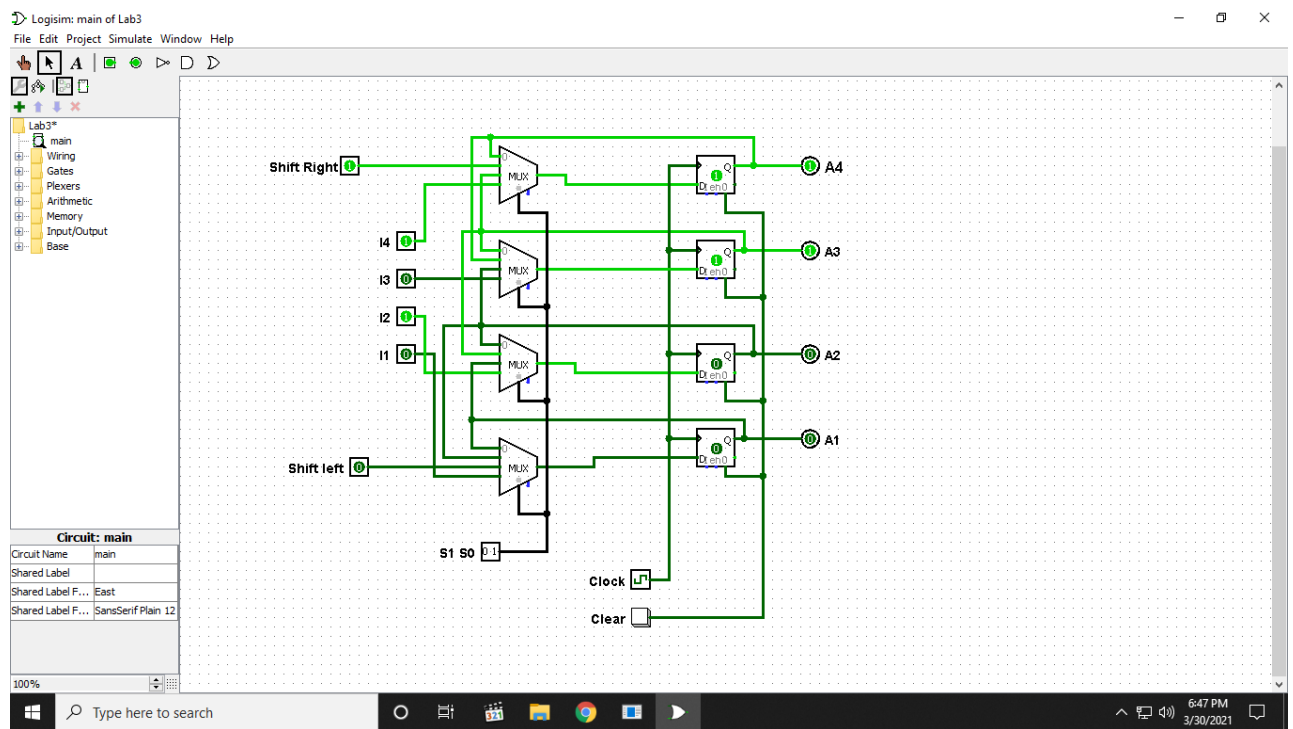

**Discussion:**

In lab 3, I construct a 4-bit Universal Shift Register. In Universal shift register there have an option to perform Shift Right when select bits are 01. When we do shift right it actually dividing by  $2^n$ . When we shift three times present bits are dividing by  $2^3$ . For left shift the current bits are multiplying by  $2^n$ . If we shift left 3 times, it means current bits multiplying by  $2^3$ . In this lab I face some theoretical problem. After understanding how this circuit works, I figure out how to do it. It took some time but finally I found out where the problem was fix the circuit and then solved it properly. By the help of our class lab instructor I fix that problem also.