

North South University
Department of Electrical & Computer Engineering

LAB REPORT

Course Name: CSE332L

Experiment Number: 01

Experiment Name: Design of a 2-bit logic unit.

Experiment Date: 03/03/2021

Report Submission Date: 10/03/2021

Faculty: SFM

Submitted to: Md Saidur RRahman

Section: 06

Student Name: **Koushik Banerjee**

Score

Student ID: **1812171642**

Remarks:


Objectives:

In this experiment, we are going to construct a 2-bit logic unit which is a part of an arithmetic logic unit (ALU). This logic unit will have 4 micro-operations which are AND, OR, XOR, and NOT operations. They can be used to change bit values, delete a group of bits or insert a new set of bits in a register. Logic micro-operations are very useful for manipulating individual bits or a portion of a word stored in a register. As we are going to design a 2-bit logic unit, we will have two outputs which are one output for each of the 2 bits.

Apparatus:

- Trainer board
- IC 7404,7408,7432,7486, 74F153 Wires for connection.

Circuit Diagram:

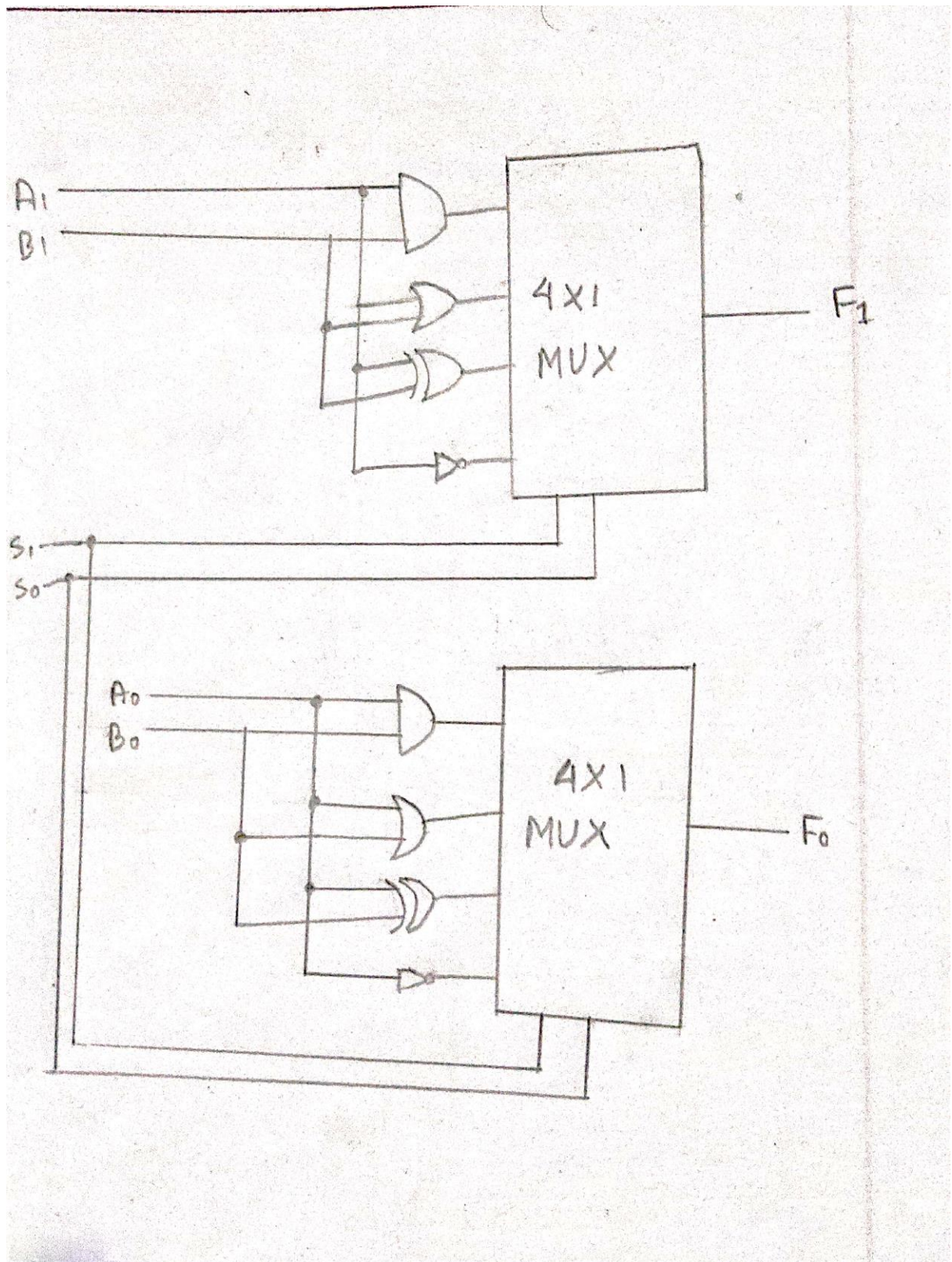


Logic Table:

A1	A0	B1	B0	AND1	AND0	OR1	OR0	XOR1	XOR0	NOT A1	NOT A0
0	0	0	0	0	0	0	0	0	0	1	1
0	0	0	1	0	0	0	1	0	1	1	1
0	0	1	0	0	0	1	0	1	0	1	1
0	0	1	1	0	0	1	1	1	1	1	1
0	1	0	0	0	0	0	1	0	1	1	0
0	1	0	1	0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1	1	1	1	0
0	1	1	1	0	1	1	1	1	0	1	0
1	0	0	0	0	0	1	0	1	0	0	1
1	0	0	1	0	0	1	1	1	1	0	1
1	0	1	0	1	0	1	0	0	0	0	1
1	0	1	1	1	0	1	1	0	1	0	1
1	1	0	0	0	0	1	1	1	1	0	0
1	1	0	1	0	1	1	1	1	0	0	0
1	1	1	0	1	0	1	1	0	1	0	0
1	1	1	1	1	1	1	1	0	0	0	0

Instruction:

- 1) Place the ICs on the trainer board.
- 2) Connect Vcc and ground to the respective pins of IC.
- 3) Connect the inputs with the switches and the outputs with LEDs.
- 4) Apply various combinations of inputs and observe the outputs.
- 5) Verify the experimental outputs with the Truth Table.


Pin configuration of ICs:

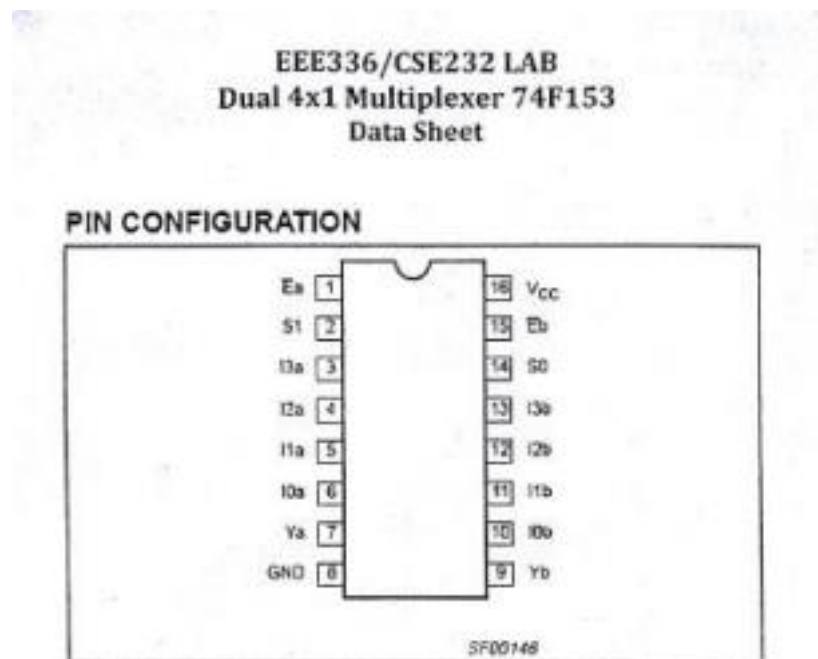

INPUT AND OUTPUT LOADING AND FAN-OUT TABLE

PINS	DESCRIPTION
I0a – I3a	Port A data inputs
I0b – I3b	Port B data inputs
S0, S1	Common Select inputs
Ea	Port A Enable input (active Low)
Eb	Port B Enable input (active Low)
Ya, Yb	Port A, B data outputs

Logisim works screenshot(s) :

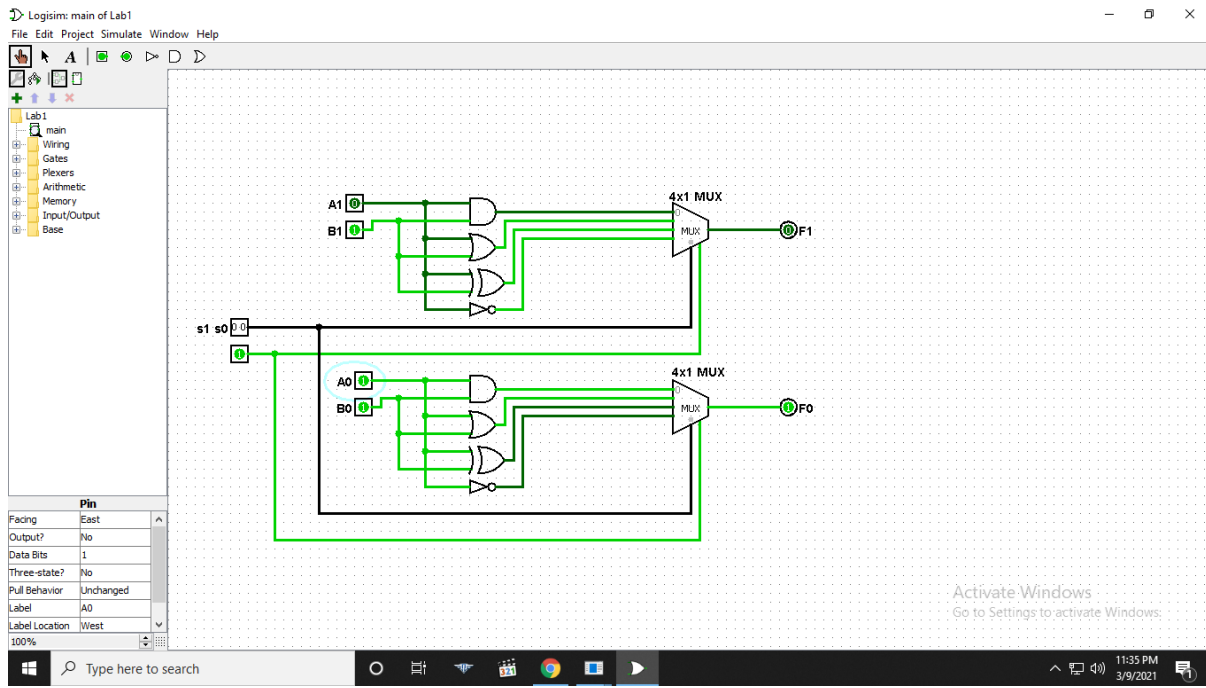

Discussion:

In lab 1 and in the lab class I face some problem doing the 4x1 MUX. I had done mistake, in min terms but I solve that by following the equation. There are 4 input, two select line, an enable key. Every component in the circuit is 2 bit. But this lab was pretty simple. It took some time but finally I found out where the problem was and fix IC circuit and then solved it properly. By the help of our class lab instructor I fix that problem also. That was all human e error problem. After understanding all the problem and practicing that problem, I answered all the questions.